



Capacitors and Inductors

W0TLM Tech Day 2023


Loren Anderson, KE0Hz

Why should you care about these?



- Don't think that this is an attempt to turn you into circuit analysis experts! We are “*simply*” going to touch on some basics and show some illustrations.
- This is fundamental technology to virtually every element of a functioning radio
 - Power supplies
 - Receiver oscillators, filters, detectors, audio amplifiers
 - Transmitter oscillators, modulators, filters, power amplifiers
 - Antennas, feedlines, impedance matching networks (tuners, baluns, RF attenuators)

Capacitors

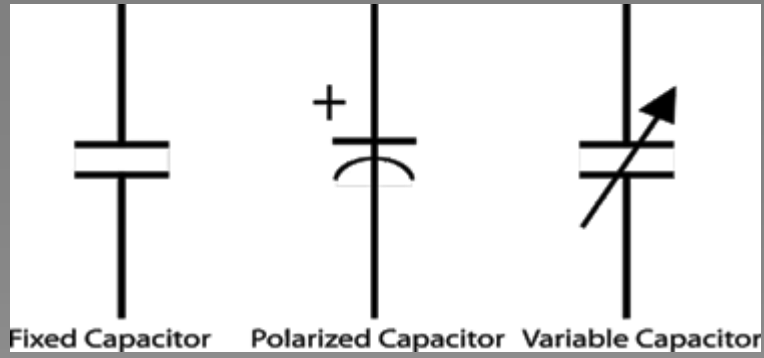

10/7/2023



W0TLM 2023 Tech Day




Characteristics of a Capacitor



- **Voltage cannot change instantaneously in a capacitor!**
- Looks like an open circuit to DC voltage
 - You may have seen the term “blocking capacitor”
- Capacitors store energy in the form of electrical charge that builds up on the capacitor’s plates
- The changing of the stored charge due when the voltage changes results in current flowing through the capacitor
 - This will be more apparent when we look at an AC circuit
- Capacitance value is a factor of the area of the plates and the *permittivity* value of the dielectric material (either air or insulating material)

Capacitors Explained

 

RC Circuit



- Applications used for circuit analysis in this presentation are


- LTSpice

<https://www.analog.com/en/design-center/design-tools-and-calculators/ltspice-simulator.html>

and

- Qspice


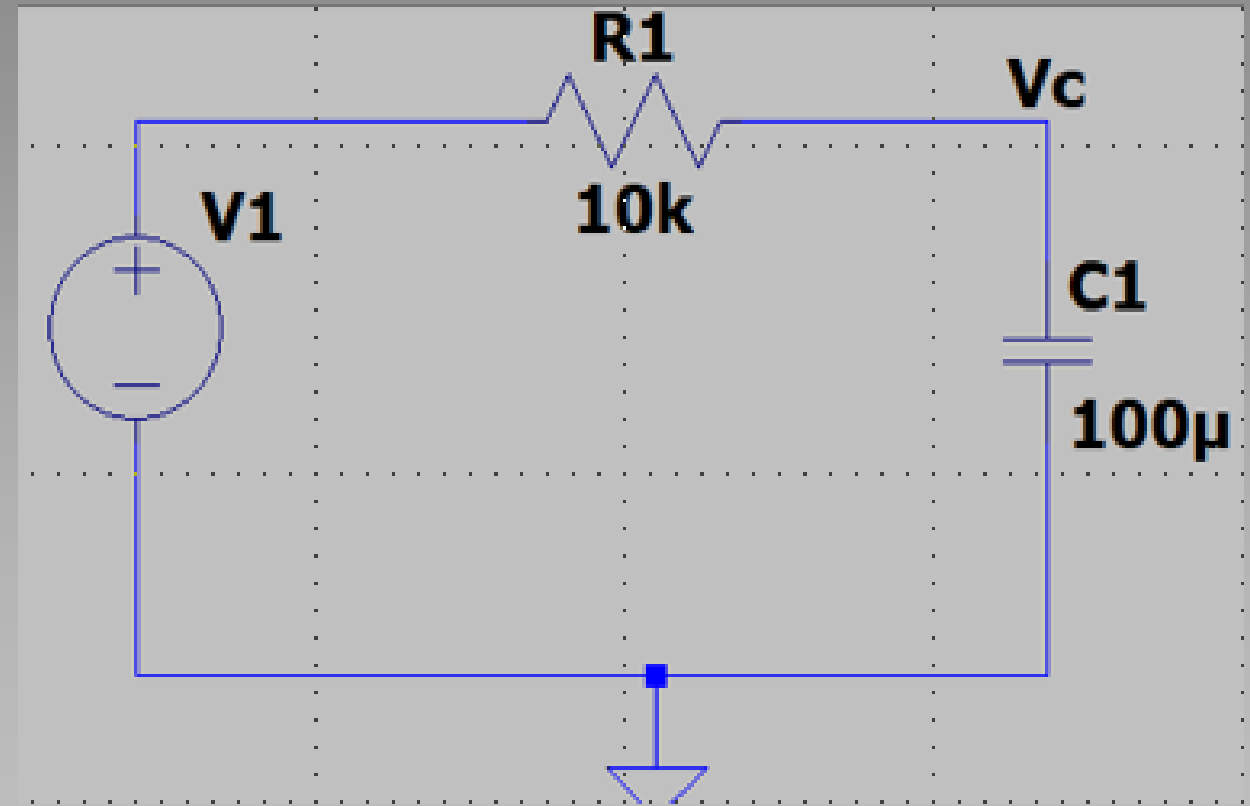
<https://www.qorvo.com/design-hub/design-tools/interactive/qspice>



Quick Aside

- The number e , also known as **Euler's number**, like π , is a mathematical constant approximately equal to 2.71828
- e is the base for the natural logarithm (ln)
- **Euler's formula**
$$e^{jx} = \cos x + j \sin x$$
- Trust the math. We don't have time to explain why!

Charging a Capacitor

  

$$V(t) = V_B(1 - e^{-t/RC}) \quad I(t) = I_0(e^{-t/RC})$$

Time Constant (τ) = RC


$$\tau = 10\text{K}\Omega \cdot 470\mu\text{F}$$

$$\tau = 4.7 \text{ s}$$




Draft1.asc Draft1.raw

Draft1.raw

 

Draft1.asc

 

Time Constant (Tau) = $RC = (10,000 \times .0001) = 1$ second



$Vc = V1(1 - e^{-t/Tau})$

@ 1 second $Vc = 1 (1 - e^{-1}) = 1 - .368 = .632V$

@ 5 seconds $Vc = 1 (1 - e^{-5}) = 1 - .006 = .993V$

.tran 10

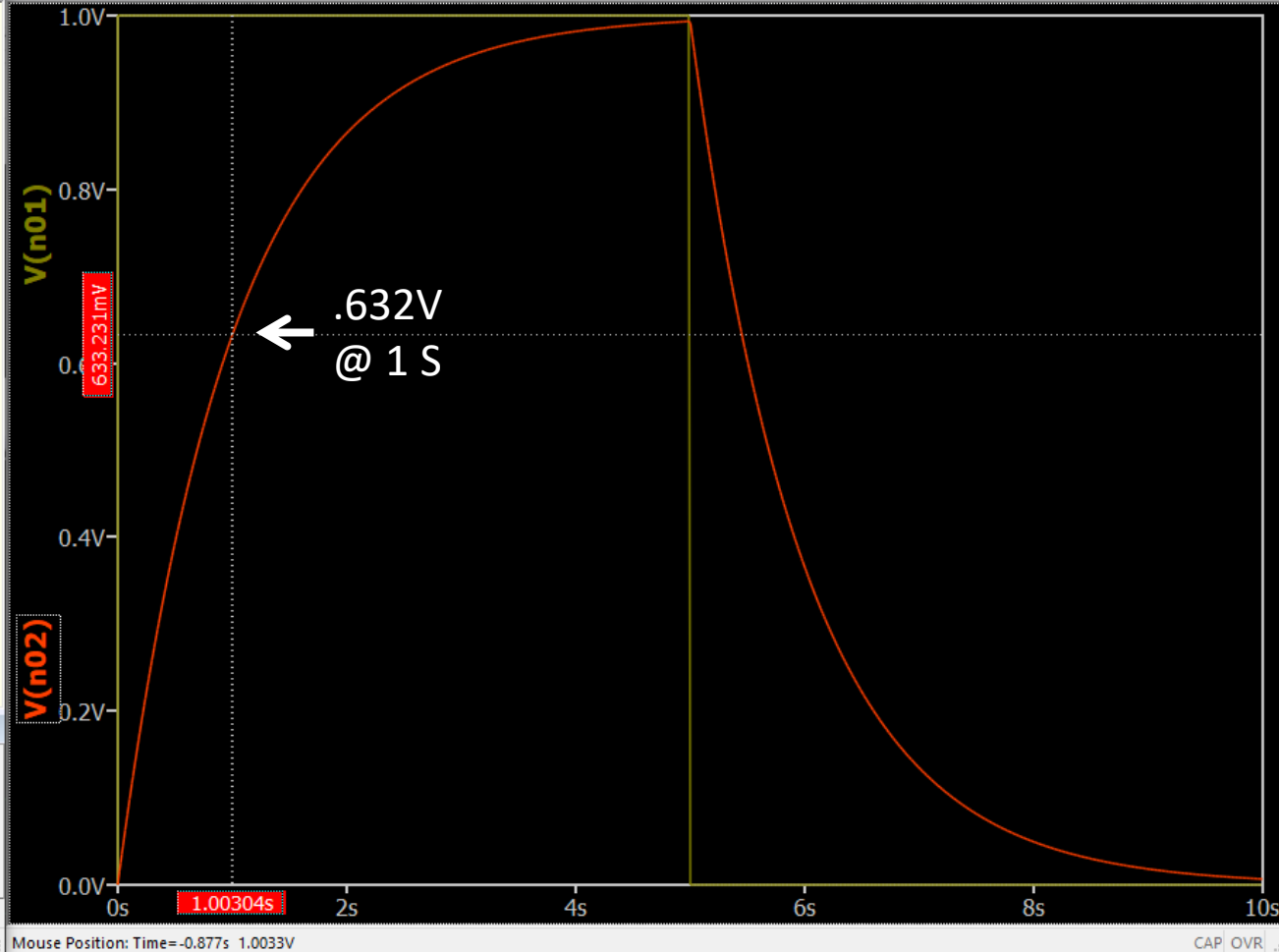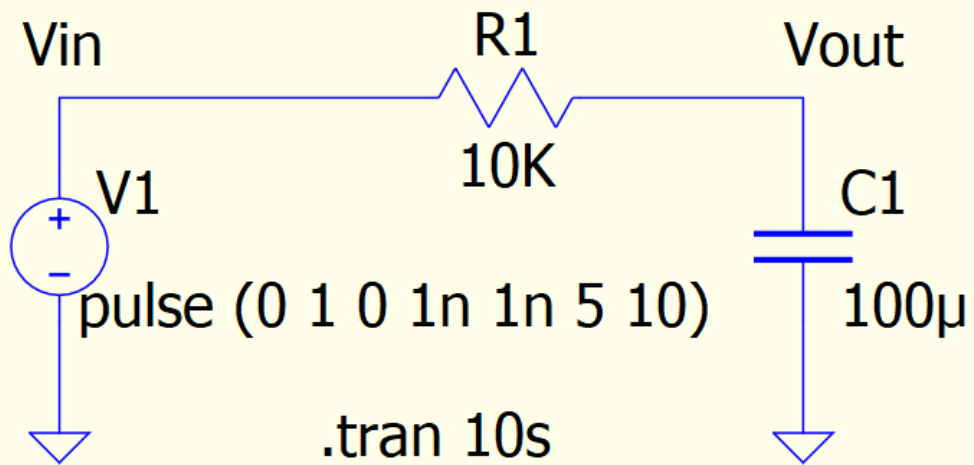10/7/2023 **PULSE(0 1 0 .0001 .0001 5 5 1)**



Time Constant (τ) = $RC = (10,000 \times .0001) = 1$ second

$V_c = V_1(1 - e^{-t/\tau})$

@ 1 second $V_c = 1(1 - e^{-1}) = 1 - .368 = .632V$

@ 5 seconds $V_c = 1(1 - e^{-5}) = 1 - .006 = .993V$

Practical uses of an RC Circuit



- AC coupling (aka DC blocking)
- Bypass (aka decoupling)
- Low pass filter
- High pass filter
- Phase shift networks
- Timing (delay) circuits
- Square wave generator (RC circuit for timing)

Capacitor values – component marking


- If a 3-digit number is present the third, non-zero number is the number of zeros that will make the number $C \times 10^{-12}$ (picofarads)
 - A capacitor marked 103 would be 10000×10^{-12} or 10000 picofarads (pf) or more commonly, .01 microfarads (.01 μf)
 - A capacitor marked 472 would be 4700 pf or .0047 μf
- If the 3-digit number ends with 0 the value is picofarads
 - A capacitor marked 220 is 220 pf

Capacitor values – on schematics

- If a polarized capacitor is required, its polarity will be marked. If not indicated assume the value to be microfarads (μf)
- Non-polarized capacitors marked with no decimal point assume to be picofarads (pf)
- Non-polarized capacitors with a decimal point assume to be microfarads (μf)

Square Wave Generator


Astable Multivibrator

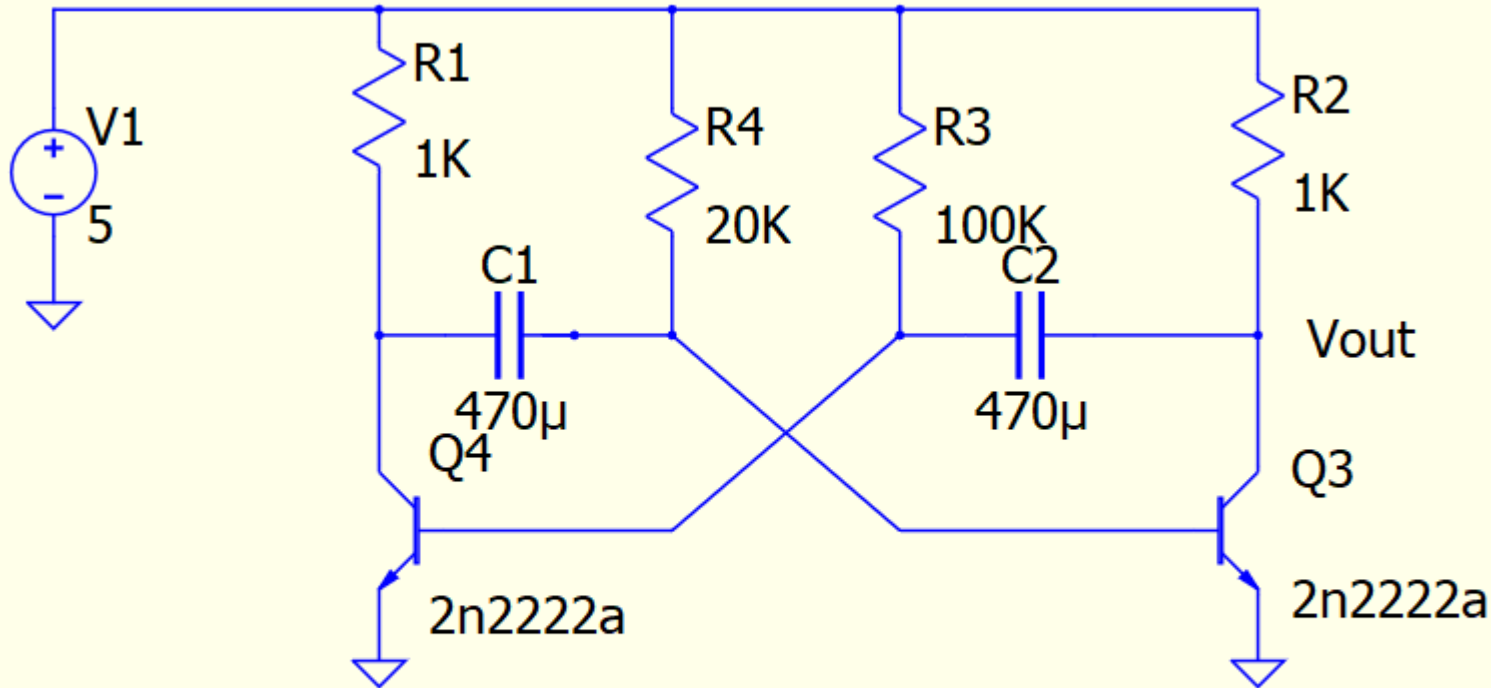

.tran 200




$$\tau_{(R4\&C1)} = RC = 20k * .00047 = 9.4 \text{ seconds}$$
 
$$\tau_{(R3\&C2)} = RC = 100k * .00047 = 47 \text{ seconds}$$




10/7/2023 Drag to move the cursor attached to "V(n05)"

Inductors

  
 


Characteristics of an Inductor

- **Current cannot change instantaneously in an inductor!**
- Inductor looks like a open circuit to DC voltage
 - Internal resistance is very low
- Inductors store energy in the form of magnetic field that occurs due to current flow
 - Inductor may or may not have a magnetic core to increase inductance (*permeability* factor)
- Voltage changes across the inductor in a circuit with changing voltage as the magnetic field changes

 

Charging an Inductor

  

$$I(t) = I_{\max} \left(1 - e^{-\frac{tR}{L}} \right) \quad V(t) = V_B \left(e^{-\frac{tR}{L}} \right)$$


$$\text{Time Constant } (\tau) = \frac{L}{R}$$

$$\tau = 15\text{H} / 10 \Omega$$

$$\tau = 1.5 \text{ s}$$

Practical Uses for RL Circuits

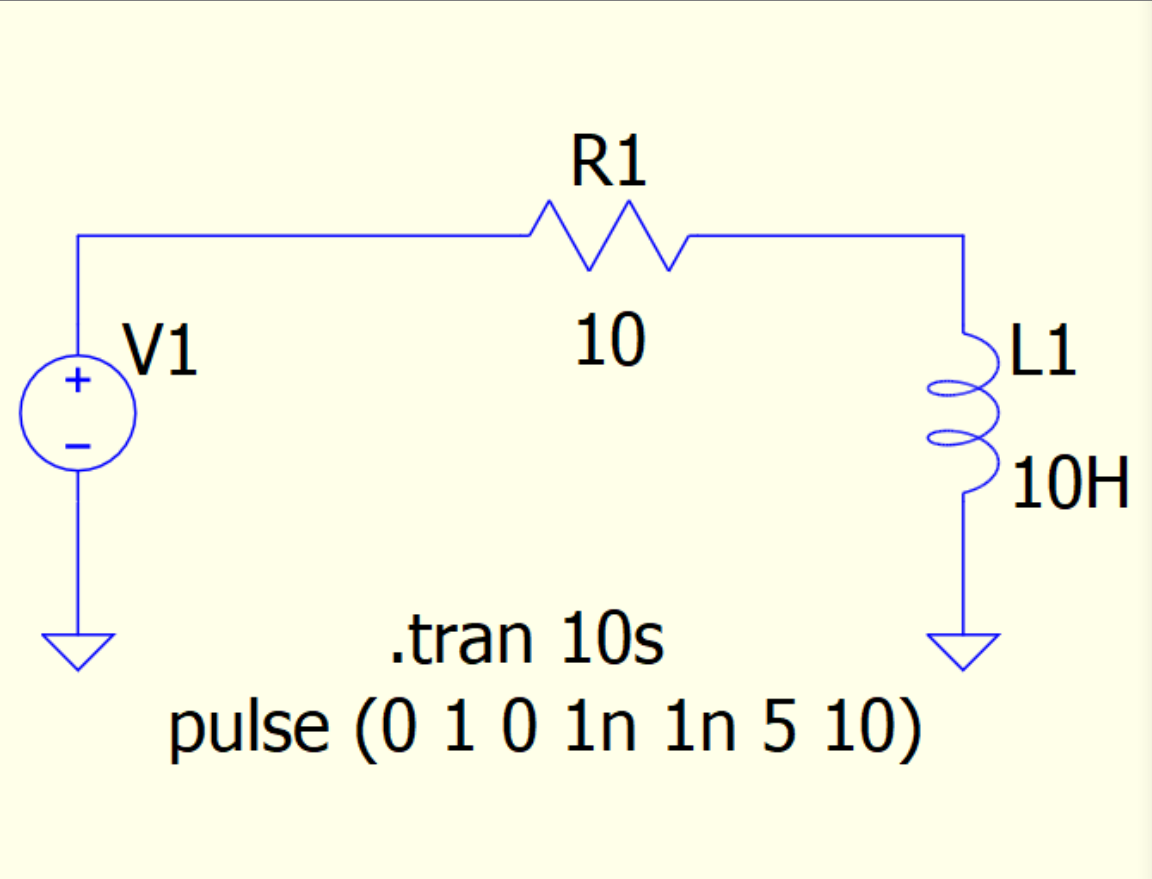- Low pass filters
- High pass filters
- Oscillator circuits
- Phase shift networks
- Voltage or current transformation
 - Baluns and transformers




Output Window

QSPICE\RLckt.qsch

Total elapsed time: 0.017799 seconds.

Simulation Post Process

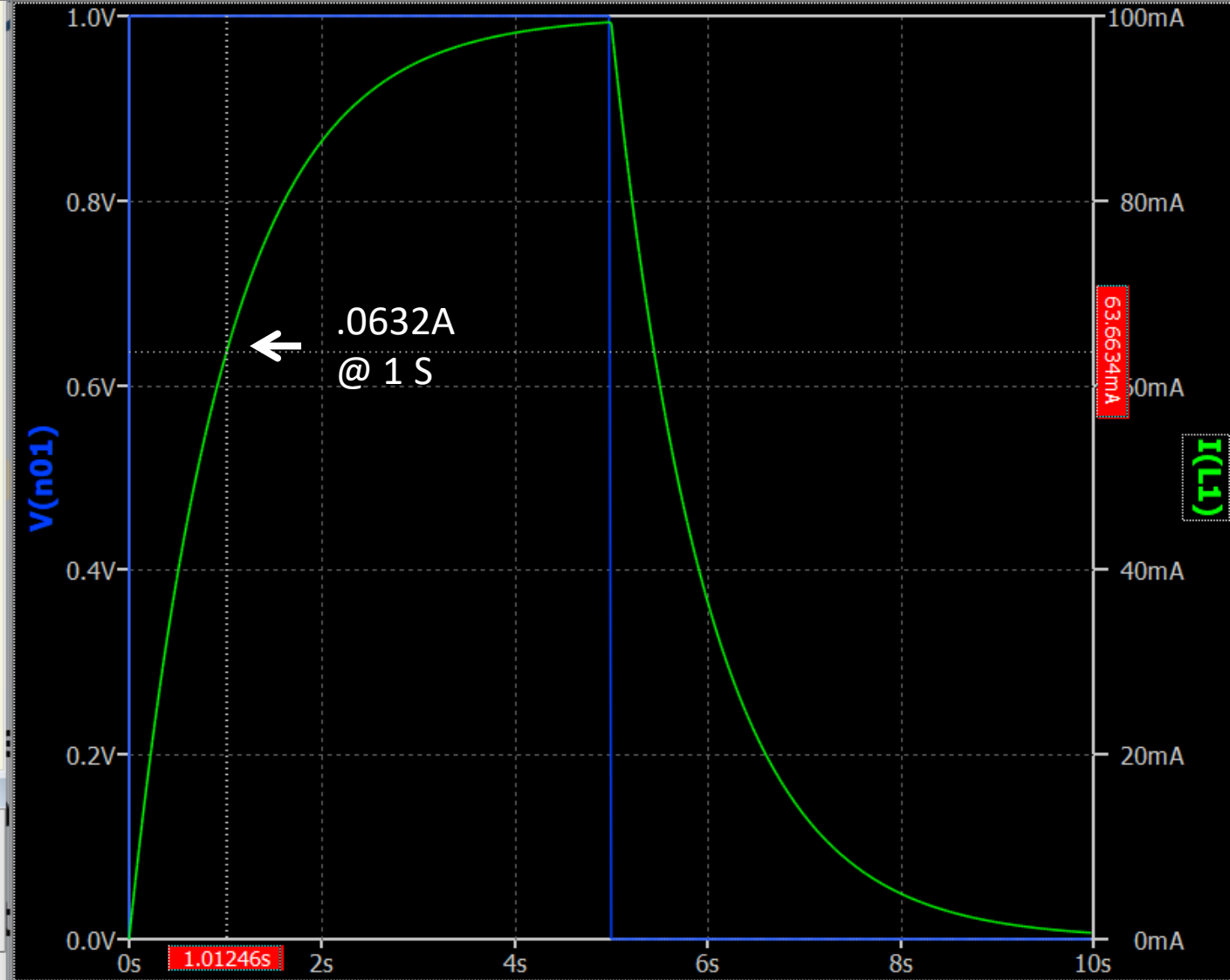

Time Constant (Tau) = $L / R = 10 / 10 = 1$ second

$I_L = (V1/R1) * (1 - e^{(-t / Tau)})$

@ 1 second $I_L = .1 * (1 - e^{-1}) = .1 - .0368 = .0632A$

@ 5 seconds $I_L = .1 * (1 - e^{-5}) = .1 - .0006 = .0993A$

Winding Inductors

- The permeability of air is ~ 1
- Toroids used by Hams are typically either powdered iron or ferrite
 - Ferrite is a ceramic material that is magnetic but non-conductive
 - Permeability is determined by the “Mix”
- The permeability of powdered iron and ferrite mixes ranges from 10 – 20,000
- The number of turns required is determined by the size of the toroid and the mix
 - The larger the toroid the more turns required for the same inductance value
 - Typically, the higher the mix number the fewer turns required
- Care must be taken to ensure the mix will support the required frequency range!

Winding Inductors

For powdered-iron cores:

$$N = 100 \frac{\sqrt{L_{\mu H}}}{A_L}$$

For ferrite cores:

$$N = 1000 \sqrt{\frac{L_{mH}}{A_L}},$$

where


N = the number of turns

$L_{\mu H}$ = inductance in microhenrys (μH)

L_{mH} = inductance in millihenrys (mH)

A_L is a property of the core material.

<http://www.electricaltechnology.org/>

 

Inductance =

$$L = (N^2 \times d^2) / (18d + 40l)$$

[inductance of air core inductor Calculator](#)

Toroid Coil Winding Calculator



Use this online tool to calculate the number of winding turns required to achieve the desired inductance

Material Type:

Iron Powder

Ferrite


Inductance

mH

Core Size

Material Number

Calculate

 

<https://66pacific.com/calculators/toroid-coil-winding-calculator.aspx>

INDUCTANCE

Desired: .1 mH

Calculated: 0.1 mH (99% of desired) Turns required: 23

CORE

Part number: FT-23-43

Frequency Range:

μ : 850

A_L : 188 mH/1000 turns







What About Phase?

Who is ELI the ICE man?

- We saw from the previous waveforms of the RC and RL circuits that the voltage across the capacitor or the current in the inductor did not change at the same time as the current or voltage changed across those components
- If the voltage source for the circuit is an AC source, regardless of frequency
 - Voltage (E) leads the current (I) in the inductor (L) (ELI)
 - Current (I) leads the voltage (E) in the capacitor (C) (ICE)
 - The amount of lead or lag depends on the frequency




Capacitor's phase shift

 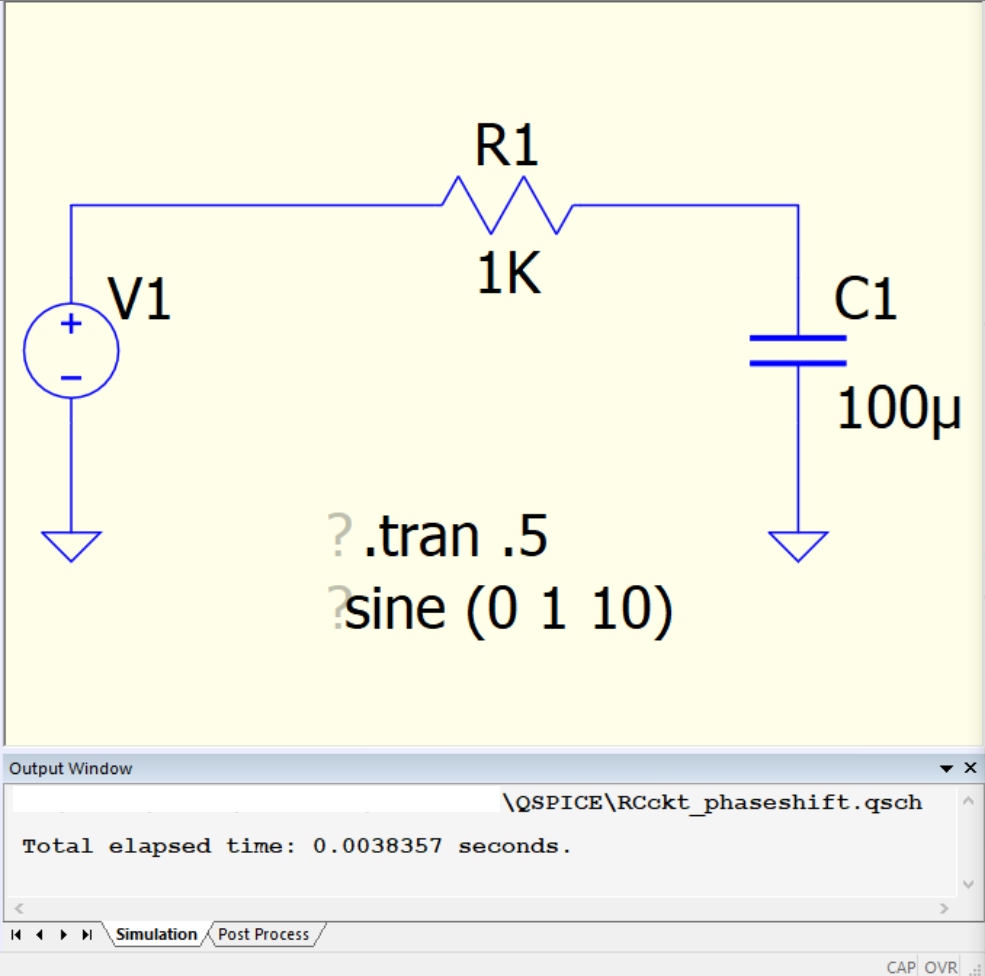


Note that the current in R1 leads the C1 voltage (ICE)

Inductor's phase shift

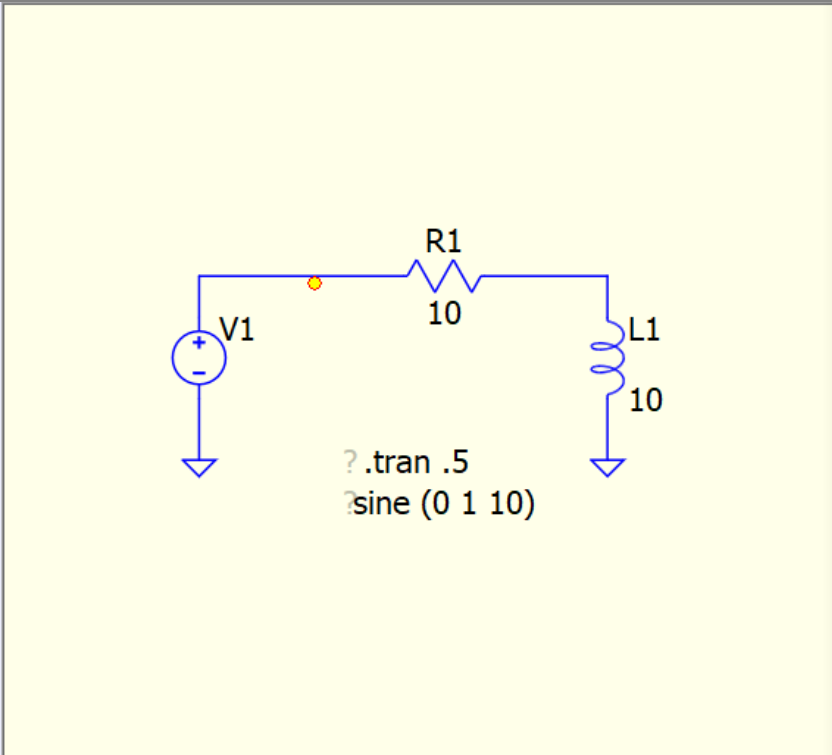

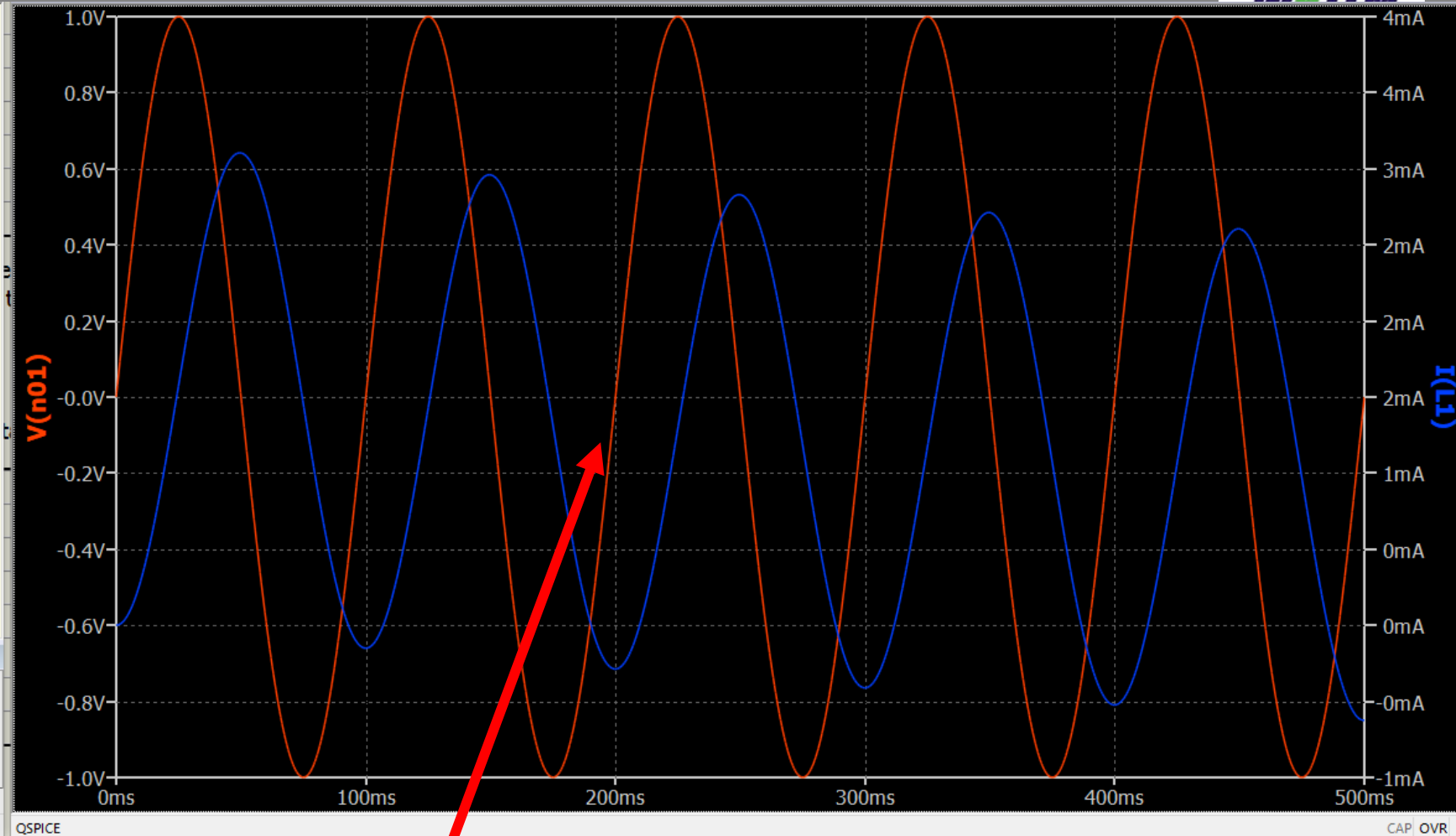Output Window
Total elapsed time: 0.0049525 seconds.



Note that the voltage leads the L1 current (ELI)

Ohm's Law applies to RLC Circuits

- Most of us are familiar with

$E = I \times R$ -> Electromotive Force (Voltage) equals Current times Resistance

- We can also write this equation as

$E = I \times Z$ -> Voltage equals Current times Impedance



- Impedance takes into consideration resistance plus the reactance of the circuit

$Z = R + jX$ (+j means inductive reactance, -j means capacitive)

- Unlike resistors, ideal capacitors and inductors don't dissipate any energy (for our purposes we'll ignore the small amounts of energy dissipated in actual devices).
- But they do have impact on circuit behavior, so we treat reactance (X) values as imaginary numbers designated by "j". Mathematicians use "i" but in electronics we don't want to confuse this with current.


What Causes Reactance?

 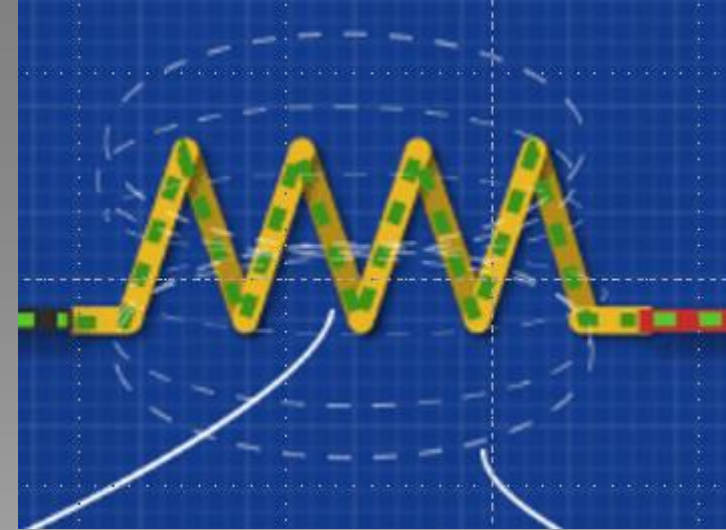- Inductive Reactance is caused by an opposition to alternating current (AC) due to an induced EMF caused by an inductor's changing magnetic field.
- Capacitive Reactance is an opposition to AC due to the EMF caused by the build up of charge across the capacitor.




Single Pole Filters


Low-Pass Filter

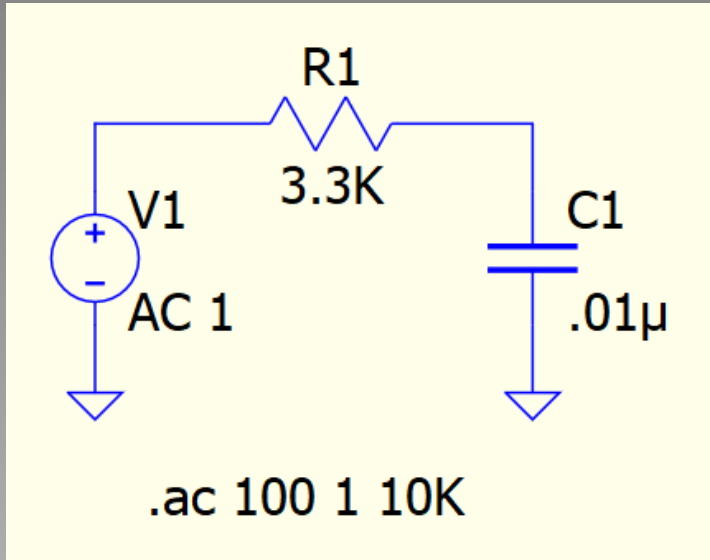

High-Pass Filter

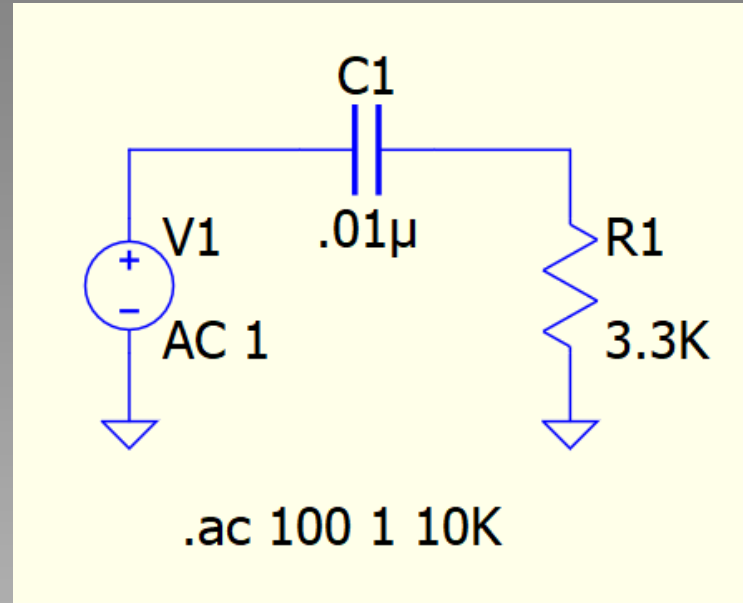

High-Pass Filter

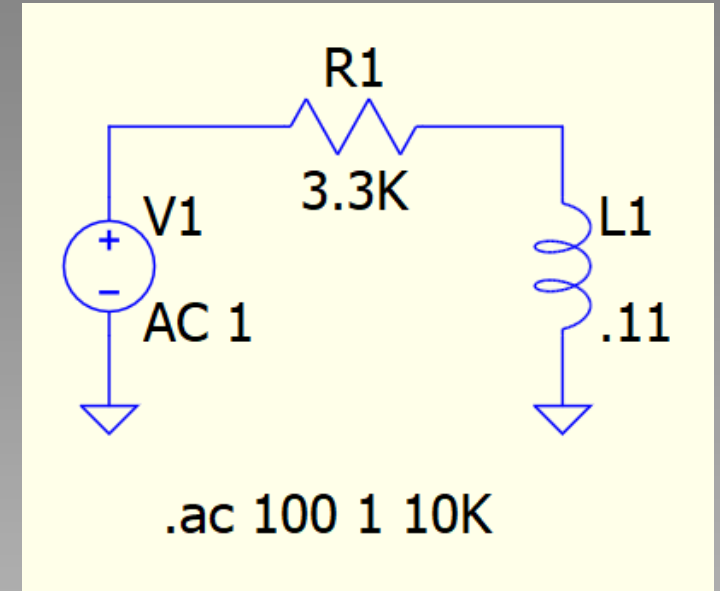

Break point of filter is identified as frequency at which output power is reduced by 3 dB (half-power point).
Think of this circuit as a divider. Half power will be at the frequency where X_C is equal to R.

$$X_C = \frac{1}{2\pi f C} = -j3.3k$$

@f = 4.823kHz


$$X_L = 2\pi f L = j3.3k$$

@f = 4.823kHz

Low-pass Filter




 
Output Window
\\QSPICE\Untitled.qsch
Total elapsed time: 0.0022754 seconds.
Simulation Post Process





.ac 100 1 10K



High-pass Filter

 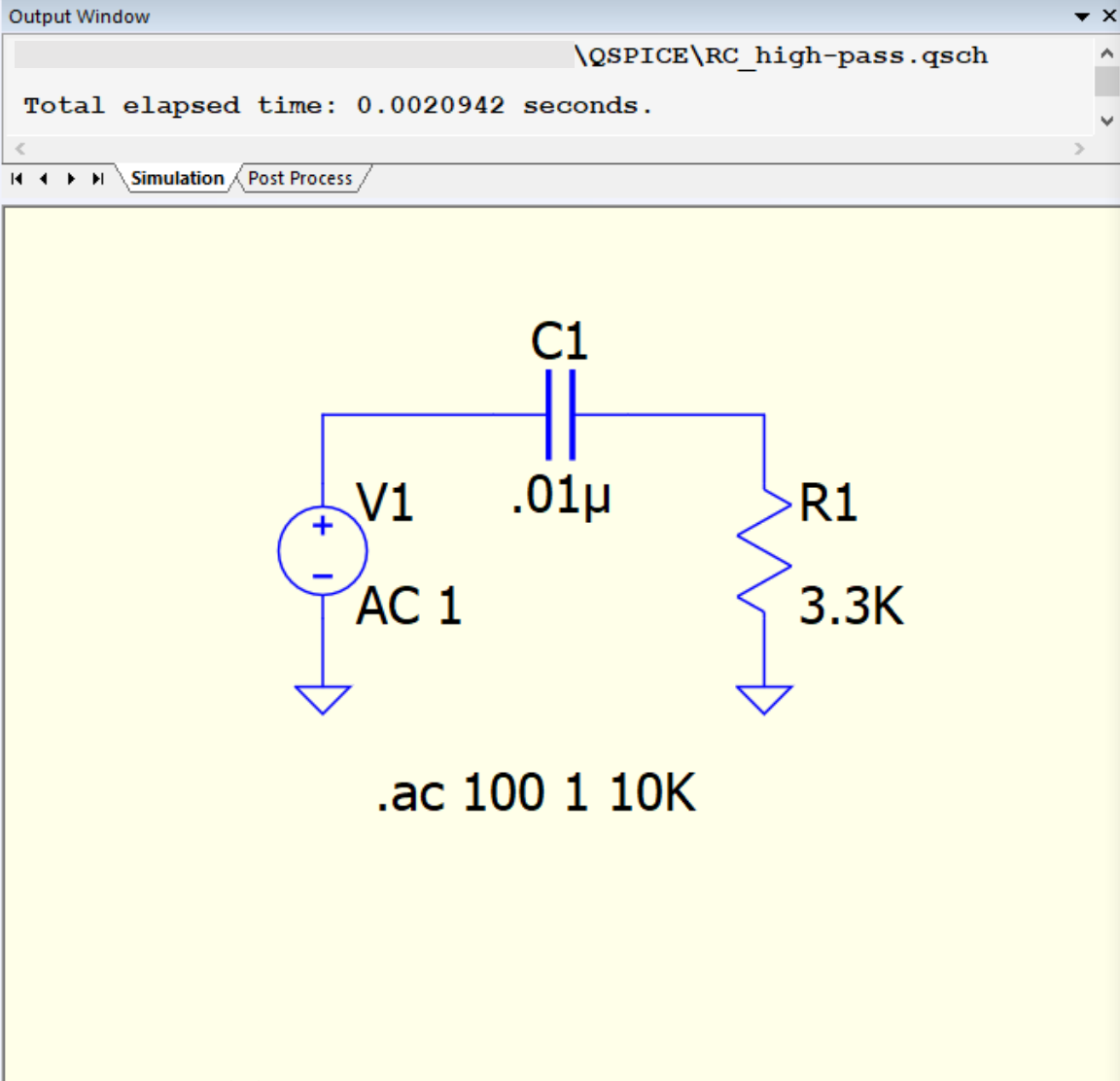


High-pass Filter

 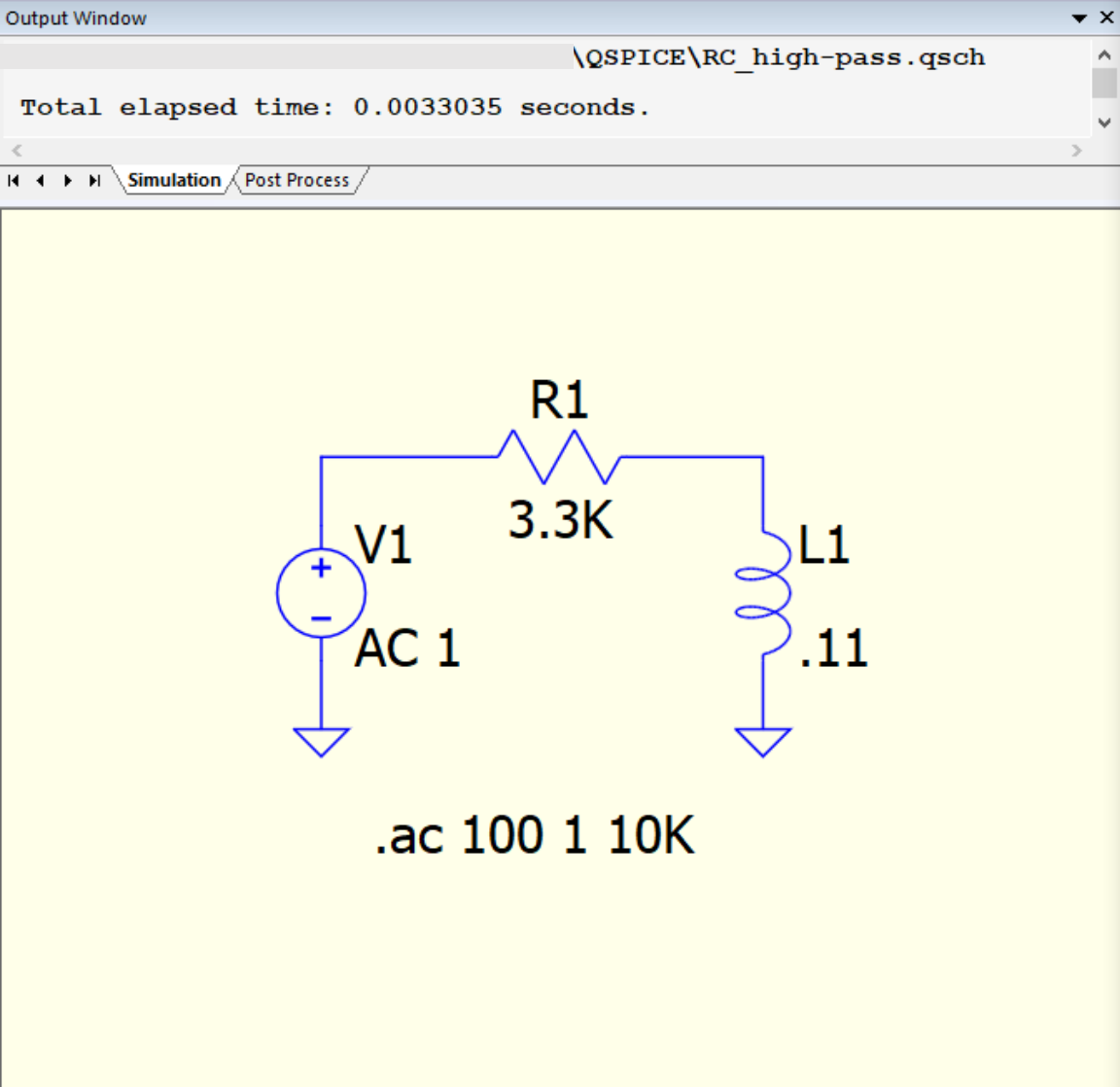

Coupling & Bypass Capacitors

Coupling capacitor (C1) - (DC Blocking)

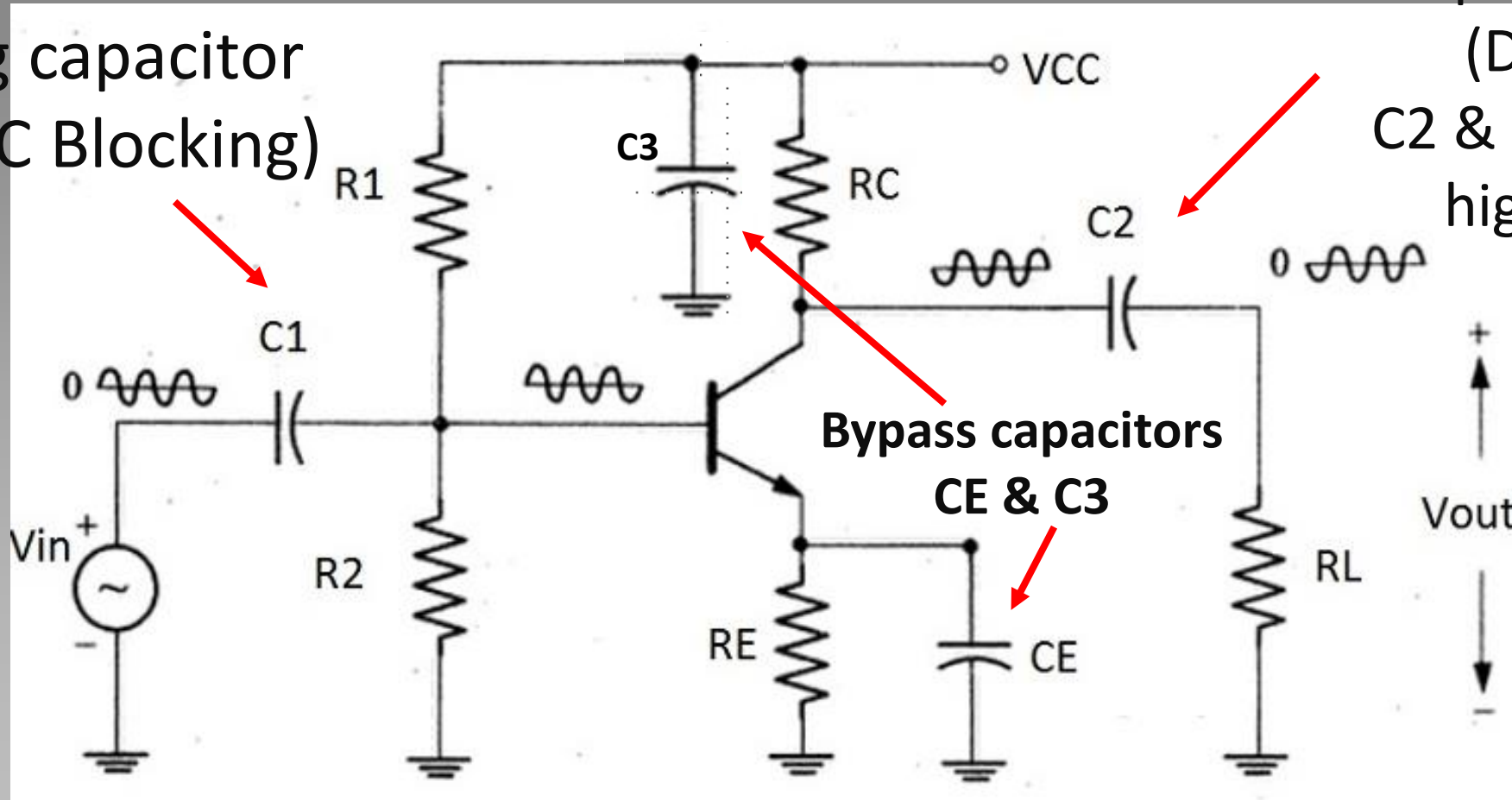Coupling capacitor (DC Blocking)
C2 & RL also act as a high-pass filter



<https://www.electronicshub.org/bypass-capacitor-tutorial/>

Coupling and Bypass Capacitors




- Bypass Capacitor - A capacitor employed to conduct AC around a component or group of components. Regularly an AC is removed from an AC/DC combination; the DC is free to pass through the bypassed component.
 - Filters AC ripple from a power source
 - Increases the AC gain in a common-emitter amplifier
- Coupling/Blocking Capacitor - A coupling capacitor is a capacitor which is used to couple or link together only the AC signal from one circuit element to another. The capacitor blocks the DC signal from entering the second element and, thus, only passes the AC signal.
 - Allows stages to have different bias voltages

Baluns/Transformers

- These are inductors configured to magnetically couple energy from a primary to secondary winding
- From Primary to Secondary
 - The voltage transformation equals the turns ratio
 - The current transformation equals the inverse of the turns ratio
 - The impedance transformation is equal to the square of the turns ratio
- In Balun (or Unun) with 1:3 turns ratio the impedance transform is 1:9 (or 50Ω:450Ω)
- There is some power lost due to heat in the toroid but most of the power is transferred.

10/7/2023
 
<http://www.radioamatoripeligni.it/i6ibe/balun9a1/balun9a1.htm>



Capacitors and Inductors in AC circuits

- Analysis becomes more complicated because reactance, unlike resistance, is frequency dependent

$$X_C = -\frac{1}{\omega C} = -\frac{1}{2\pi fC}$$

$$X_L = \omega L = 2\pi fL$$

- In an RC circuit $Z = R - jX_C$
- In an RL circuit $Z = R + jX$